

Last time

- Finished two's comp.
- Start circuits & logic

Today

- Truth tables
- Logic gates
- Circuits
 - construction
 - DNF, CNF
- Logical Equivalence
 - Laws of Boolean algebra
- Logical Completeness
- Circuits for addition
 - half-adder
 - full-adder
 - ripple-carry adder

Next time

- Propositional & Predicate Logic

Motivating example: binary addition

$$\begin{array}{l} \text{a: } \\ \text{b: } \\ \hline \end{array}$$

$$\begin{array}{r} 1 0 1 \\ + 1 1 0 \\ \hline 1 0 1 1 \end{array}$$

$$\begin{array}{r} 1 1 1 \\ + 1 0 1 \\ \hline 1 1 0 0 \end{array}$$

Carry

sum



$(a_0 = 0 \text{ AND } b_0 = 1) \text{ OR } (a_0 = 1 \text{ AND } b_0 = 0)$
 $(a_0 = \text{NOT } 1 \text{ AND } b_0 = 1) \text{ OR } (a_0 = 1 \text{ AND } b_0 = \text{NOT } 1)$

a_0	b_0	s_0
0	0	0
0	1	1
1	0	1
1	1	0

a_0	b_0	c_0
0	0	0
0	1	0
1	0	0
1	1	1

truth tables

Boolean function

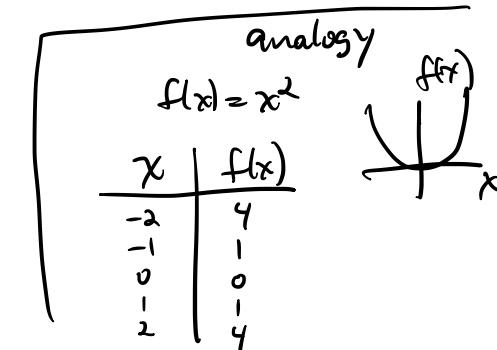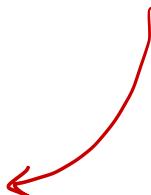

AND, OR, NOT

a	b	<u>a AND b</u>
0	0	0
0	1	0
1	0	0
1	1	1

$a \wedge b$, $a \cdot b$, $a \Rightarrow b$


Digression: Switches



normally open




normally closed
push to open

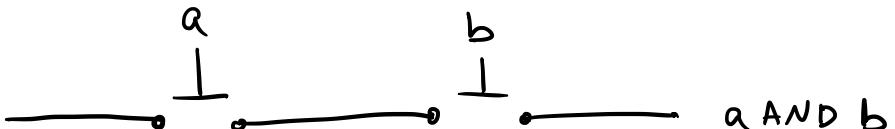

0	0V	F	no current open
1	+5V	T	current closed

OR

a	b	a OR b
0	0	0
0	1	1
1	0	1
1	1	1

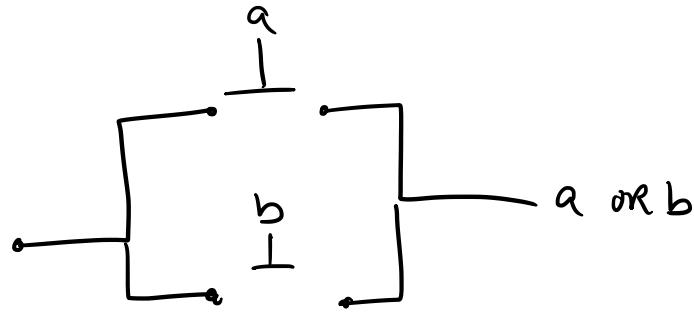


OR, +, $a \vee b$



NOT

a	NOT A
0	1
1	0

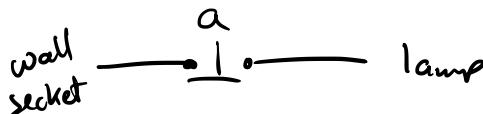

NOT, $\neg a$, \bar{a}



Laws of (Boolean) Logic/Algebra

comm.
law

normal algebra

$$a+b = b+a$$

$$a \cdot b = b \cdot a$$

:

Boolean algebra

$$a \vee b = b \vee a$$

$$a \wedge b = b \wedge a$$

dist.

$$a \cdot (b+c) = a \cdot b + a \cdot c$$

$$p \wedge (q \vee r) = (p \wedge q) \vee (p \wedge r)$$

$$p \vee (q \wedge r) = (p \vee q) \wedge (p \vee r)$$

ident.

$$a \cdot 1 = a$$

$$p \wedge T = p$$

$$a + 0 = a$$

$$p \vee F = p$$


De Morgan

$$\neg(p \wedge q) = \neg p \vee \neg q$$

$$\neg(p \vee q) = \neg p \wedge \neg q$$

a	b	out
0	0	1
0	1	1
1	0	0
1	1	1

DNF construction

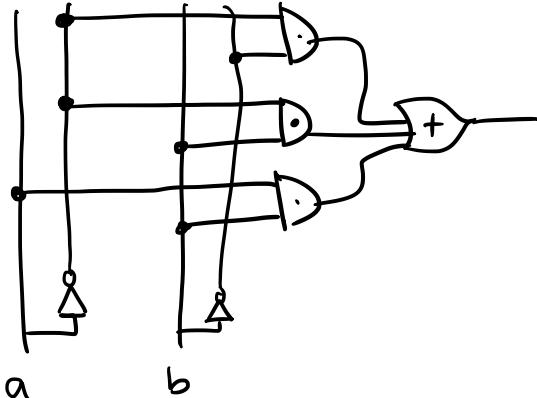

$$\equiv (\neg a \wedge \neg b) \vee (\neg a \wedge b) \vee (a \wedge b)$$

?

$$\equiv \neg a \vee b$$

a	b	$\neg a \vee b$
0	0	1
0	1	1
1	0	0
1	1	1

Example (Logical Equivalence)

$$(\neg a \wedge \neg b) \vee [(\neg a \wedge b) \vee (a \wedge b)]$$

$$\equiv (\neg a \wedge \neg b) \vee ((\neg a \vee a) \wedge b)$$

$$\equiv (\neg a \wedge \neg b) \vee (\top \wedge b)$$

$$\equiv (\neg a \wedge \neg b) \vee b$$


$$\equiv (\neg a \vee b) \wedge (\neg b \vee b)$$

$$\equiv (\neg a \vee b) \wedge \top$$

$$\equiv \neg a \vee b$$

$NAND$

a	b	$a \text{ NAND } b$
0	0	1
0	1	1
1	0	1
1	1	0

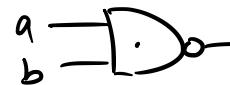

XOR

a	b	$a \text{ XOR } b$
0	0	0
0	1	1
1	0	1
1	1	0



(+)

$a \oplus b$